

UG 3rd Semester Examination 2021

Computer Science (General)

Paper- SEC-1

Digital System Design

[CBCS]

Full Marks: 32

Time: 2Hours

(The figure in the margin indicate full marks)

Group-A

1. Answer any *six* questions: 2 X 6 = 12
- a) $(3412)_8 = (?)_{10}$
 - b) What is gray code?
 - c) Implement NAND and OR gate using NOR gate.
 - d) What is latch?
 - e) Simplify the following expression: $(A+B)(A+C) + A$
 - f) Why MUX is known as Data Selector?
 - g) What is edge triggering?

Group-B

Answer any *two* questions

10 X 2 = 20

2. a) Differentiate between Minterm and Maxterm. Convert the following expression to its equivalent maxterm expression: $A' + AB'C + ABC'$. 2+3=5
- b) State and prove De Morgan's Theorem in Boolean algebra. 5
3. a) What is Decoder? Draw the circuit diagram of a 2 X 4 decoder. 2+3=5
- b) Solve the function using K-Map method: 5
- $f(A,B,C) = \sum(1,2,4,5,6)$
4. a) Describe SR flip-flop with its circuit diagram. 5
- b) What is race-around condition? How it is solved? 2+3=5